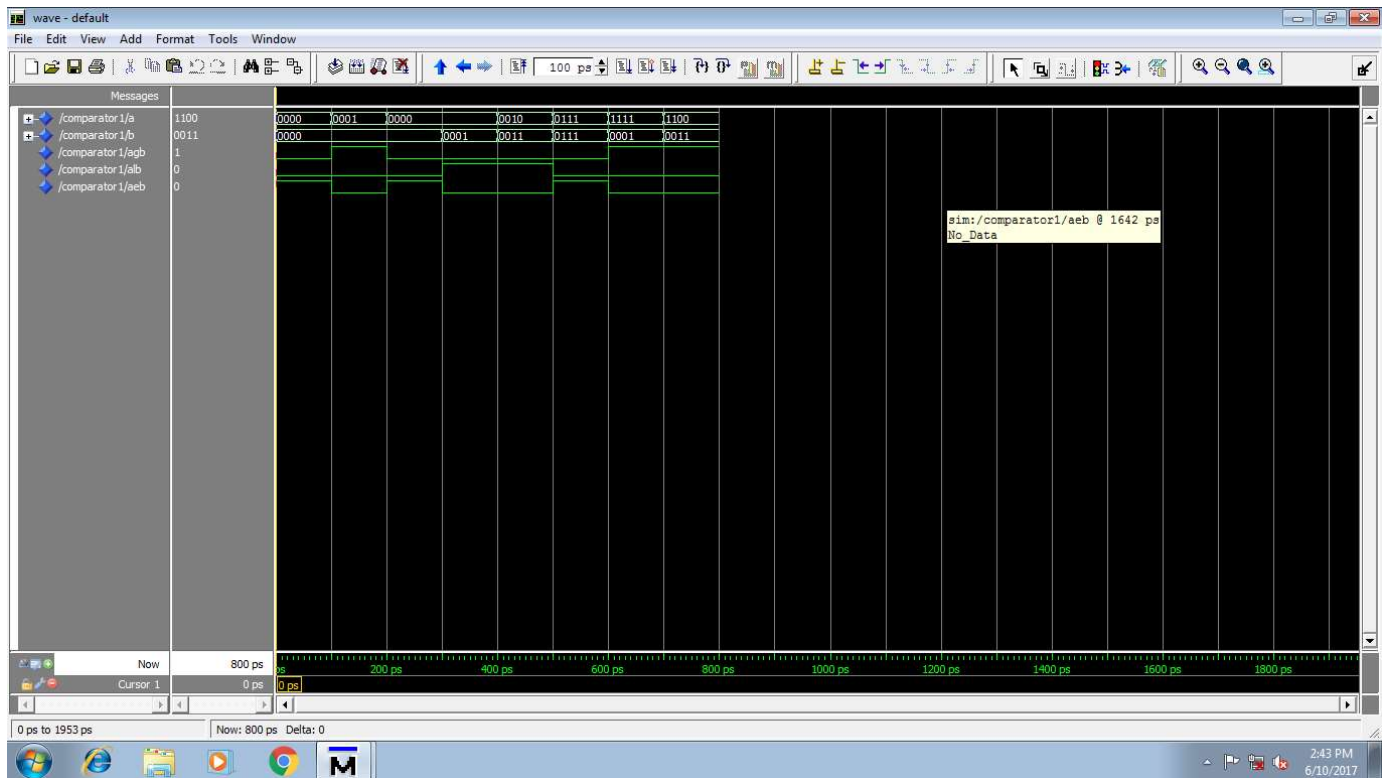


- Please edit the code for priority encoder 8:3 before you write, upload the same, and send a pull request
- Also, please add the output for 8:1 MUX

4 bit Comparator Behavioral



library ieee;

```
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
```

entity comparator1 is

```
port(
    a,b : in std_logic_vector(3 downto 0);
    agb : out std_logic;
    alb : out std_logic;
    aeb : out std_logic
);
```

end comparator1;

architecture comp_arch of comparator1 is

```
begin
```

```
    process (a,b)
```

```
    begin
```

```
        if a>b then
```

```
            agb <= '1';
```

Thank You For Your Help. Please mail to abhishekmadhu.uem@gmail.com if you make the said changes.


- Please edit the code for priority encoder 8:3 before you write, upload the same, and send a pull request
- Also, please add the output for 8:1 MUX

```

alb <= '0';
aeb <= '0';
elsif a<b then
  agb <= '0';
  alb <= '1';
  aeb <= '0';
else
  aeb <= '1';
  alb <= '0';
  agb <= '0';
end if;
end process;
end comp_arch;

```

4 bit Comparator DataFlow

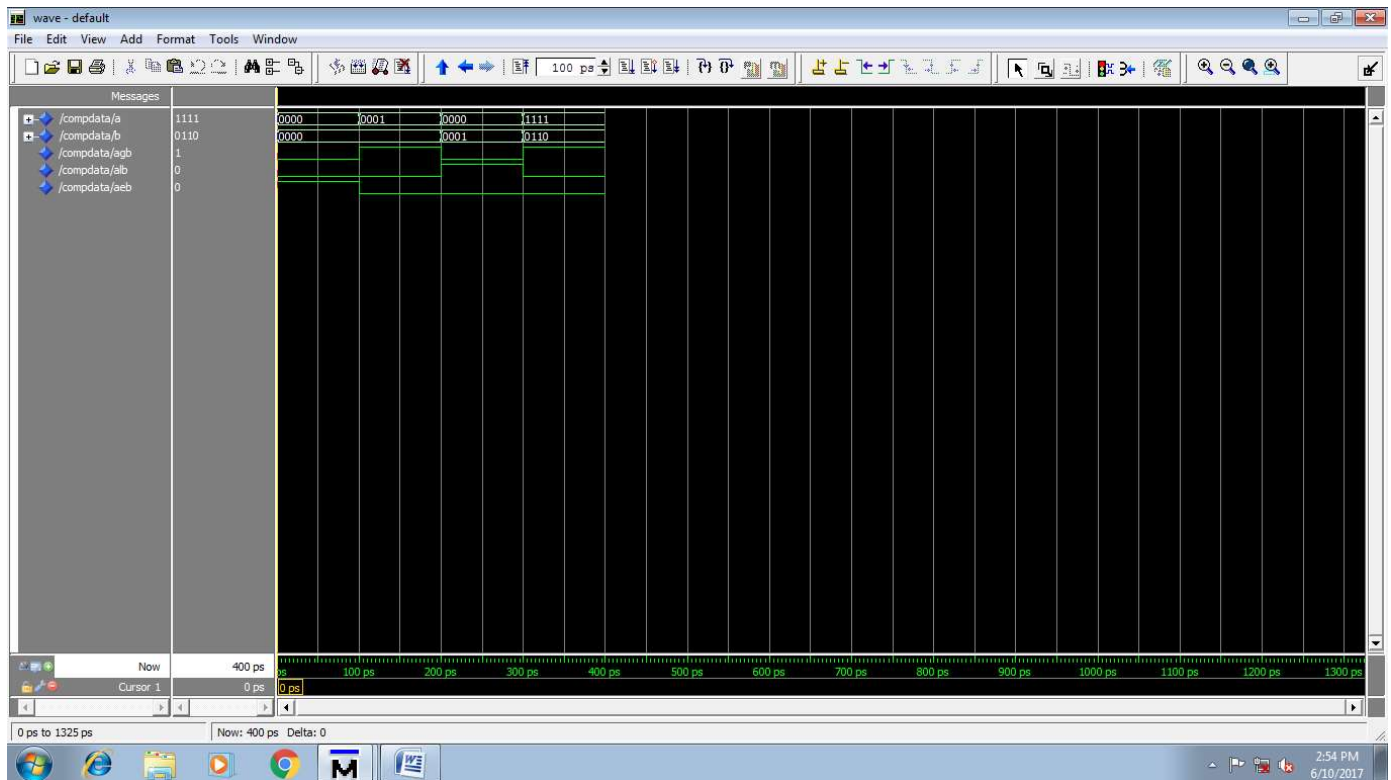

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

```

Thank You For Your Help. Please mail to abhishekmadhu.uem@gmail.com if you make the said changes.

- Please edit the code for priority encoder 8:3 before you write, upload the same, and send a pull request
- Also, please add the output for 8:1 MUX

entity CompData is

```
port(
  a,b : in std_logic_vector(3 downto 0);
  agb : out std_logic;
  alb : out std_logic;
  aeb : out std_logic;
);
```

end CompData;

architecture data_arch of CompData is

begin

```
  agb <= '1' when (a>b)
```

```
  else '0';
```

```
  alb <= '1' when (a<b)
```


```
  else '0';
```

```
  aeb <= '1' when (a=b)
```

```
  else '0';
```

```
end data_arch;
```

2-BIT Comparator Behavioral

 

Thank You For Your Help. Please mail to abhishekmadhu.uem@gmail.com if you make the said changes.

- Please edit the code for priority encoder 8:3 before you write, upload the same, and send a pull request
- Also, please add the output for 8:1 MUX


```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity TBBComp is
port(
    a,b : in std_logic_vector(1 downto 0);
    agb : out std_logic;
    alb : out std_logic;
    aeb : out std_logic
);
end TBBComp;
architecture comp_arch2 of TBBComp is
begin
    process (a,b)
    begin
        if a>b then
            agb <= '1';
            alb <= '0';
            aeb <= '0';
        elsif a<b then
            agb <= '0';
            alb <= '1';
            aeb <= '0';
        else
            aeb <= '1';
            alb <= '0';
            agb <= '0';
        end if;
    end process;
end comp_arch2;
```

2 bit comparator using DataFlow

Thank You For Your Help. Please mail to abhishekmadhu.uem@gmail.com if you make the said changes.

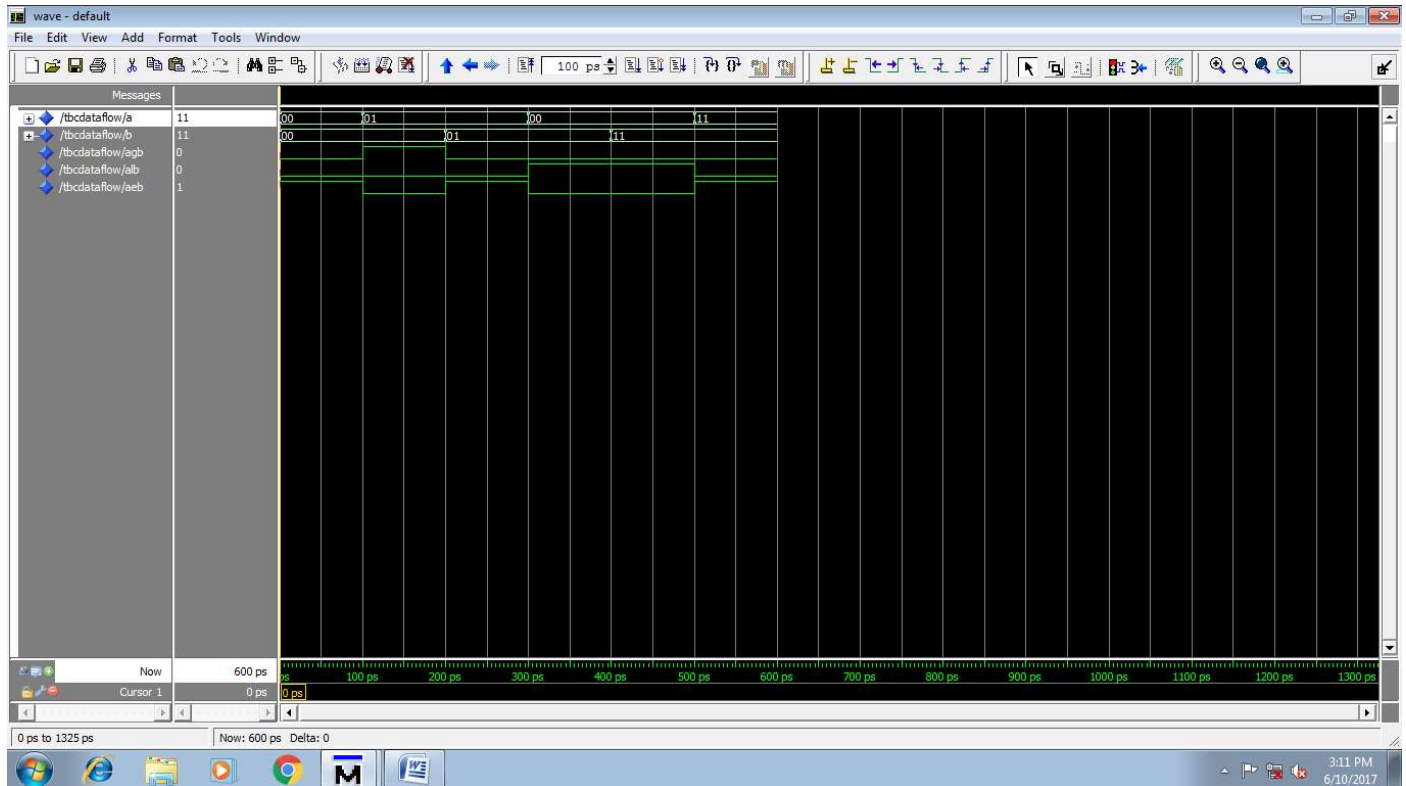- Please edit the code for priority encoder 8:3 before you write, upload the same, and send a pull request
- Also, please add the output for 8:1 MUX



library ieee;

```
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
```

entity TBCDataflow is

```
port(
    a,b : in std_logic_vector(1 downto 0);
    agb : out std_logic;
    alb : out std_logic;
    aeb : out std_logic
);
```

end TBCDataflow;

architecture data_arch4 of TBCDataflow is


```
begin
    agb <= '1' when (a>b)
    else '0';
    alb <= '1' when (a<b)
    else '0';
    aeb <= '1' when (a=b)
    else '0';
```

Thank You For Your Help. Please mail to abhishekmadhu.uem@gmail.com if you make the said changes.

- Please edit the code for priority encoder 8:3 before you write, upload the same, and send a pull request
- Also, please add the output for 8:1 MUX

end data_arch4;

Priority Encoder 4:2

 

library ieee;

```
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
```

entity FXTPEnc is

```
port(
    a : in std_logic_vector(3 downto 0);
    b : out std_logic_vector(1 downto 0)
);
```

end FXTPEnc;

architecture data_arch5 of FXTPEnc is

begin

process (a)

begin

if (a="0001") then

b <= "00";

Thank You For Your Help. Please mail to abhishekmadhu.uem@gmail.com if you make the said changes.

- Please edit the code for priority encoder 8:3 before you write, upload the same, and send a pull request
- Also, please add the output for 8:1 MUX

```

        elsif (a = "0010") then
            b<= "01";

        elsif (a>"0010" and a<"0100") then
            b <= "01";

        elsif (a = "0100") then
            b<= "10";

        elsif (a>"0100" and a<"1000") then
            b <= "10";

        elsif (a="1000" or a>"1000") then
            b <= "11";

    end if;
end process;
end data_arch5;

```

Priority Encoder 8:3

Incomplete code:

```

library ieee;

use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity EXTPEnc is
    port(
        a : in std_logic_vector(7 downto 0);
        b : out std_logic_vector(2 downto 0)
    );
end EXTPEnc;

architecture data_arch6 of EXTPEnc is
    begin
        process (a)
            begin
                if (a="00000001") then
                    b <= "000";

                elsif (a = "00000010") then

```

Thank You For Your Help. Please mail to abhishekmadhu.uem@gmail.com if you make the said changes.

- Please edit the code for priority encoder 8:3 before you write, upload the same, and send a pull request
- Also, please add the output for 8:1 MUX

```

b<= "001";

elseif (a>"00000010" and a<"00000100") then
    b <= "001";
    ---C
elseif (a = "00000100") then
b<= "001";

elseif (a>"00000100" and a<"00001000") then
    b <= "010";
    ---C
elseif (a = "00000010") then
b<= "010";

elseif (a>"00000010" and a<"00000100") then
    b <= "010";
    ---
elseif (a = "00000010") then
b<= "011";

elseif (a>"00000010" and a<"00000100") then
    b <= "011";
    ---
elseif (a = "00000010") then
b<= "100";

elseif (a>"00000010" and a<"00000100") then
    b <= "100";
    ---
elseif (a = "00000010") then
b<= "101";

elseif (a>"00000010" and a<"00000100") then
    b <= "101";
    ---
elseif (a = "00000010") then
b<= "110";

```

Thank You For Your Help. Please mail to abhishekmadhu.uem@gmail.com if you make the said changes.

- Please edit the code for priority encoder 8:3 before you write, upload the same, and send a pull request
- Also, please add the output for 8:1 MUX

```


elseif (a>"00000010" and a<"00000100") then
    b <= "110";
---
elseif (a = "00000010") then
    b<= "111";

elseif (a>"00000010" and a<"00000100") then
    b <= "111";
---

end if;
end process;
end data_arch6;

```

MUX 4:1

 

```

library ieee;
use ieee.std_logic_1164.all;

```

Thank You For Your Help. Please mail to abhishekmadhu.uem@gmail.com if you make the said changes.

- Please edit the code for priority encoder 8:3 before you write, upload the same, and send a pull request
- Also, please add the output for 8:1 MUX

```
--use ieee.std_logic_arith.all;
--use ieee.std_logic_unsigned.all;
```

```
entity MUX_4to2 is
```

```
  port(
    A,B,C,D,S0,S1 : in std_logic;
    Z : out std_logic
  );
end MUX_4to2;
```

```
architecture bhv_MUX of MUX_4to2 is
```

```
  begin
    process(A,B,C,D,S0,S1)
    begin
      if(S0 = '0' and S1 = '0') then
        Z<=A;
      elsif(S0='0' and S1='1') then
        Z<=B;
      elsif(S0='1' and S1='0') then
        Z<=C;
      elsif(S0='1' and S1='1') then
        Z<=D;
      end if;
    end process;
  end bhv_MUX;
```

MUX 8:3

```
library ieee;
```

```
  use ieee.std_logic_1164.all;
  --use ieee.std_logic_arith.all;
  --use ieee.std_logic_unsigned.all;
```

```
entity MUX_4to2 is
```

```
  port(
    A,B,C,D,E,F,G,H,S0,S1,S2 : in std_logic;
    Z : out std_logic
  );
end MUX_4to2;
```

Thank You For Your Help. Please mail to abhishekmadhu.uem@gmail.com if you make the said changes.

- Please edit the code for priority encoder 8:3 before you write, upload the same, and send a pull request
- Also, please add the output for 8:1 MUX

architecture bhv_MUX of MUX_4to2 is

```
begin
  process(A,B,C,D,S0,S1)
  begin
    if(S0 = '0' and S1 = '0' and S2='0') then
      Z<=A;
    elsif(S0='0' and S1='0' and S2='1') then
      Z<=B;
    elsif(S0='0' and S1='1' and S2='0') then
      Z<=C;
    elsif(S0='0' and S1='1' and S2='1') then
      Z<=D;
    elsif(S0 = '1' and S1 = '0' and S2='0') then
      Z<=E;
    elsif(S0='1' and S1='0' and S2='1') then
      Z<=F;
    elsif(S0='1' and S1='1' and S2='0') then
      Z<=G;
    elsif(S0='1' and S1='1' and S2='1') then
      Z<=H;
    end if;
  end process;
end bhv_MUX;
```

Please Run this code and find the output.

Thank You For Your Help. Please mail to abhishekmadhu.uem@gmail.com if you make the said changes.